## Exercise 8: Sort it out!

## Task 1: Associative or not Associative?

- a) Provide the truth table of  $\diamond_M$ .
- b) Show that  $\diamond_M$  is associative. Using a computer program is fine, as long as you provide clear and well-documented code and structure the output in a readable form.
- c) Show that there is an associative operator  $\{0,1\}^2 \to \{0,1\}$  whose closure is not associative! (Hint: There are not too many candidates, and quite a few can be ruled out easily. However, using a computer makes the search trivial!)

## Task 2: Is it a CMUX?

- a) Provide a small circuit implementing  $\diamond_M$ . (Hint: If you can do c) right away, you can skip a), but you can score points for a) if c) proves challenging.)
- b) Provide a small circuit implementing out<sub>M</sub>. (Hint: As for a).)
- c) Provide a small circuit that can be used to compute each bit of either function (changing to which wires the inputs go and negating inputs or outputs to the circuit is fine).

## Task 3\*: Too much Detail?

- a) One can provide smaller implementations of a CMUX when working on the transistor level. Find out about this!
- b) Can you provide efficient transistor-level implementations of the subcircuits implementing  $\diamond_M$  and  $\operatorname{out}_M$ ?
- c) Induce a flow of information to your fellow students in the TA session!