 


Phase Locked Loops, PLLs, for Clocking Chips







Ian W. Jones
and
Felipe A. Kuentzer





ianjones@mpi-inf.mpg.de
kuentzer@ihp-microelectronics.com
December 2020

Outline




Part 1:

-  Overview
-  Intro to PLLs
-  Clocking with PLLs
-  Analog PLLs

Part 2:





-  Recap
-  Digital PLLs
-  Future challenges
-  Summary

Recap





-  Clocked chips => ease design (uniformity)
-  PLLs
 - => low jitter, stable
 - => programmable
 - => ratioed phase-related clocks
 - => enable many forms of data communication
-  Analog PLLs => excellent, but:
large & high power

Outline

Part 1:


-  Overview
-  Intro to PLLs
-  Clocking with PLLs
-  Analog PLLs

Part 2:

-  Recap
-  **Digital PLLs**
-  Future challenges
-  Summary


Analog PLL
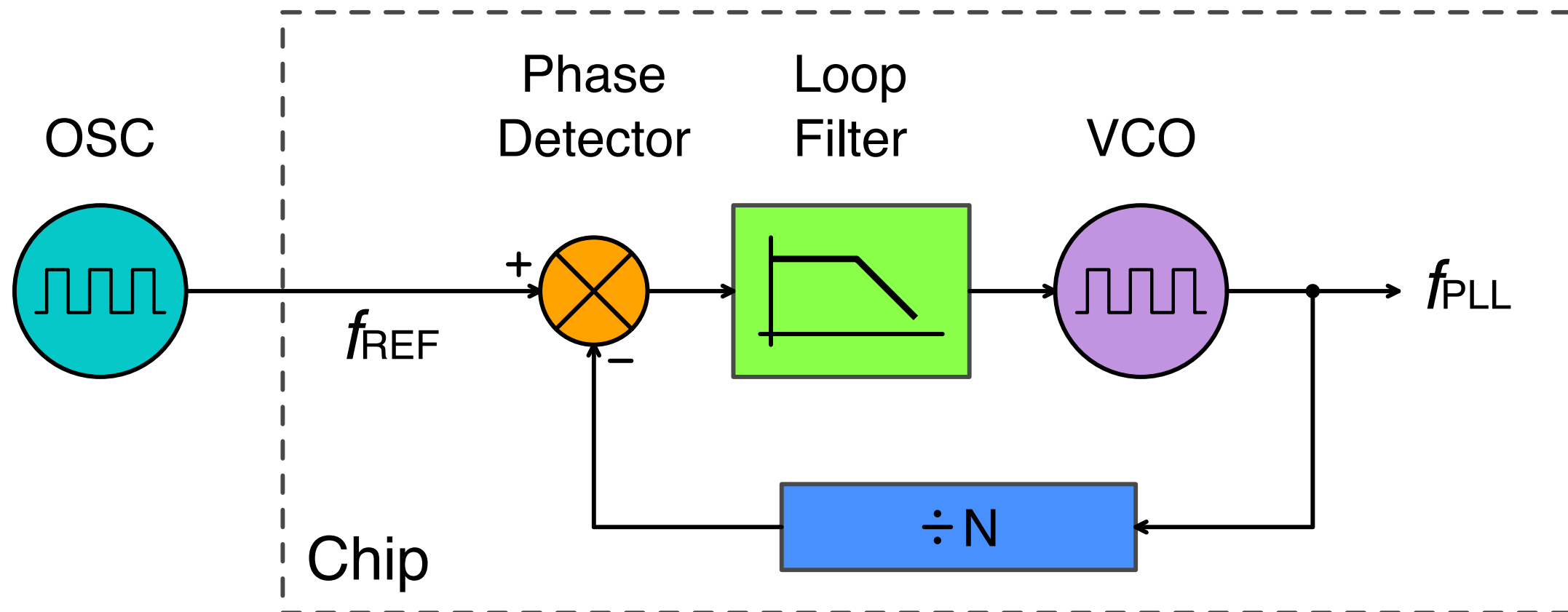
$$f_{\text{PLL}} = N \times f_{\text{REF}}$$




Digital PLL
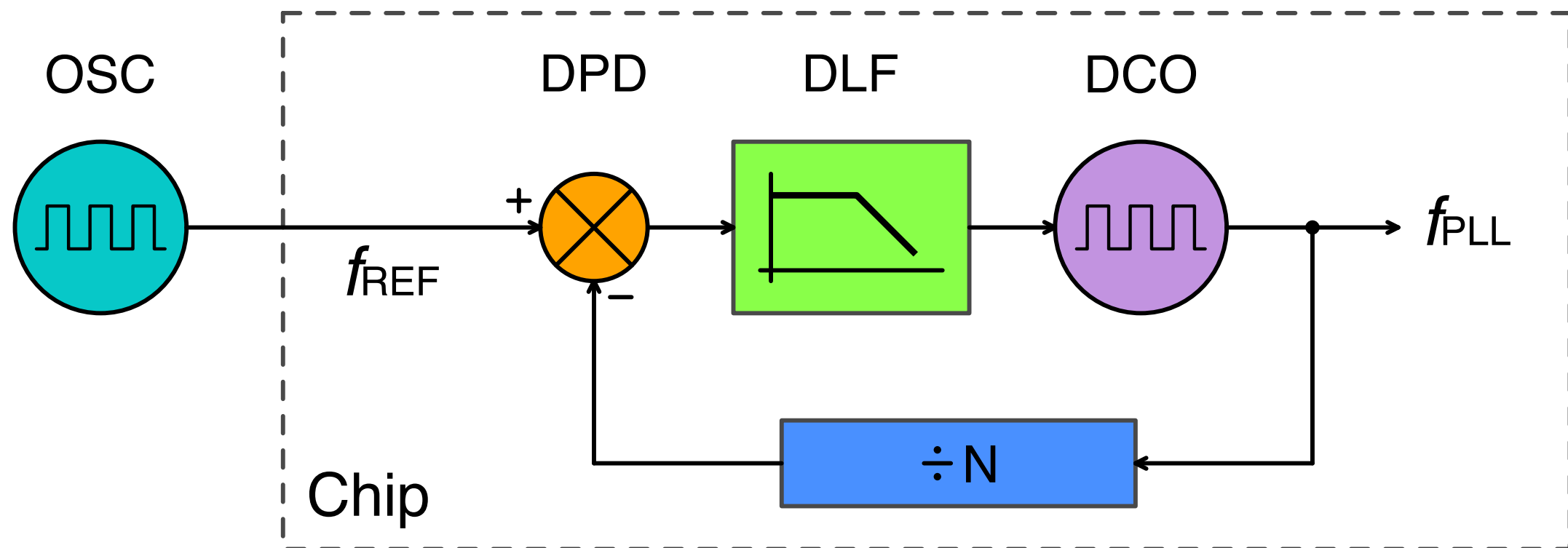
$$f_{\text{PLL}} = N \times f_{\text{REF}}$$



Digital PLL Components

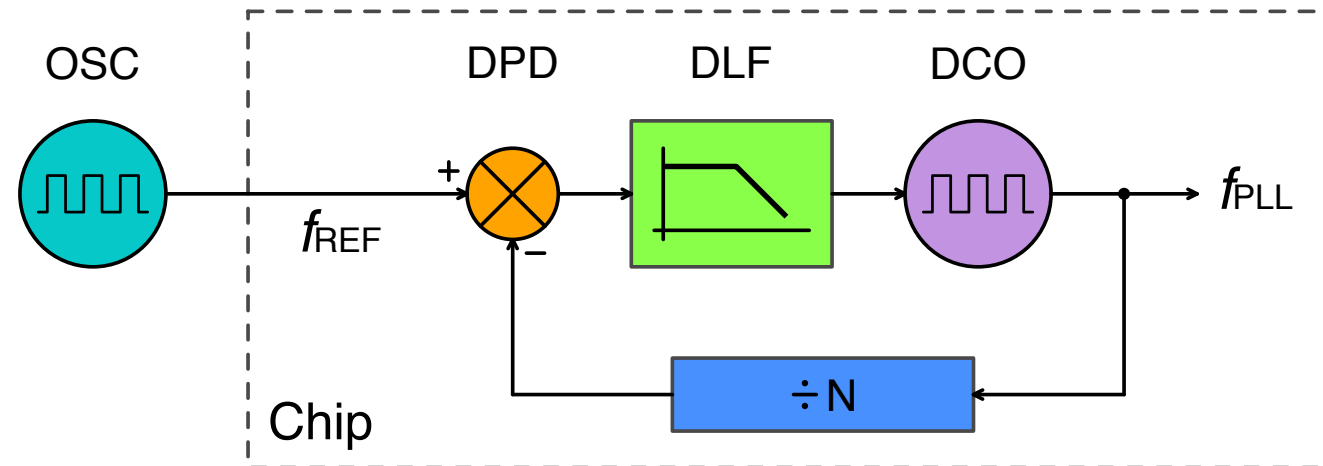

OSC

– External clock reference

DCO

– On-chip Digital Controlled Oscillator


DPD

– Digital Phase Detector

DLF

– Digital Loop Filter

Digital PLL Components

 

OSC

– External clock reference

DCO

– On-chip Digital Controlled Oscillator



DPD

– Digital Phase Detector



DLF

– Digital Loop Filter


Digital Controlled Oscillator, DCO

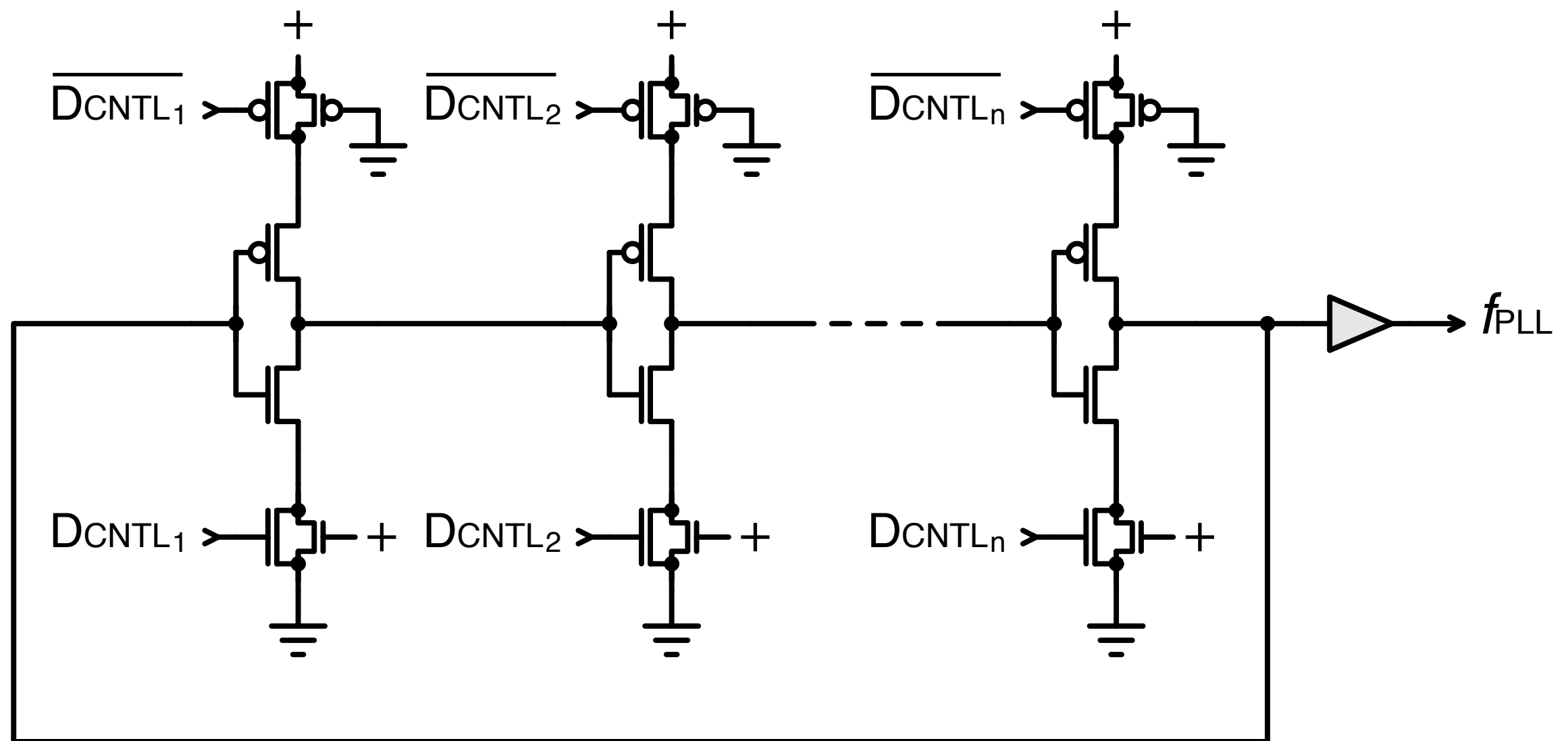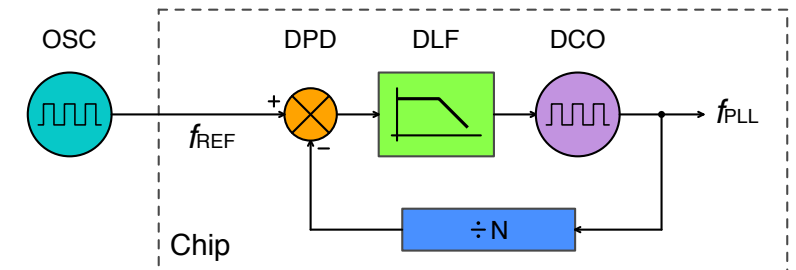

Digital Controlled Oscillator, DCO

  

Digital PLL Components

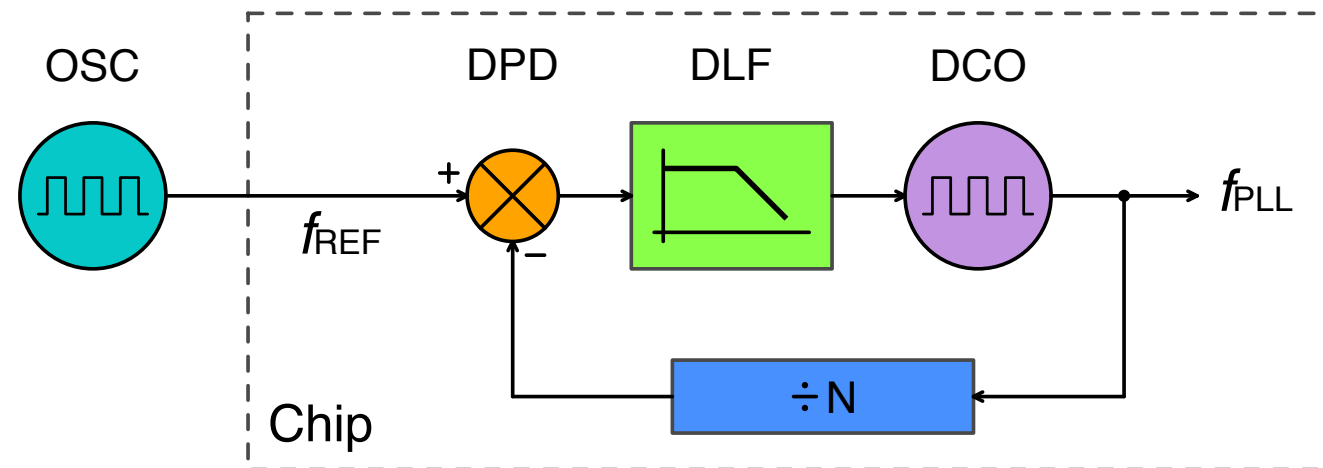

OSC

– External clock reference

DCO

– On-chip Digital Controlled Oscillator


DPD

– Digital Phase Detector


DLF

– Digital Loop Filter

Digital Phase Detector, DPD


 


Time-To-Digital Converter, TDC:

 



Digital Phase Detector, DPD

TDC waveforms:

  


Digital Phase Detector, DPD

TDC steps:

  

Digital PLL Components

 

OSC

– External clock reference

DCO

– On-chip Digital Controlled Oscillator

DPD



– Digital Phase Detector

DLF


– Digital Loop Filter

Digital Loop Filter, DLF


4-stage FIR low-pass filter:

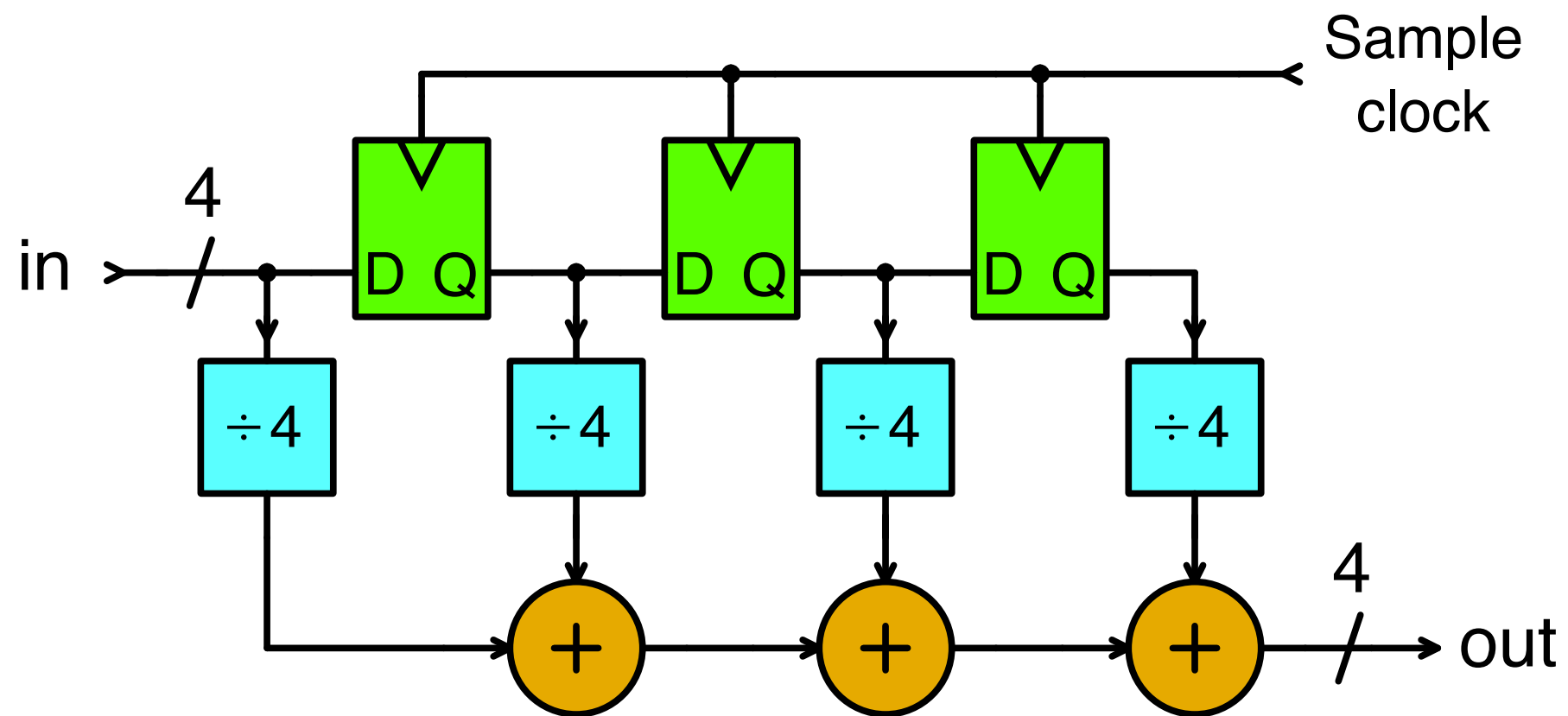 

Digital PLL

 


Discussion Session #1

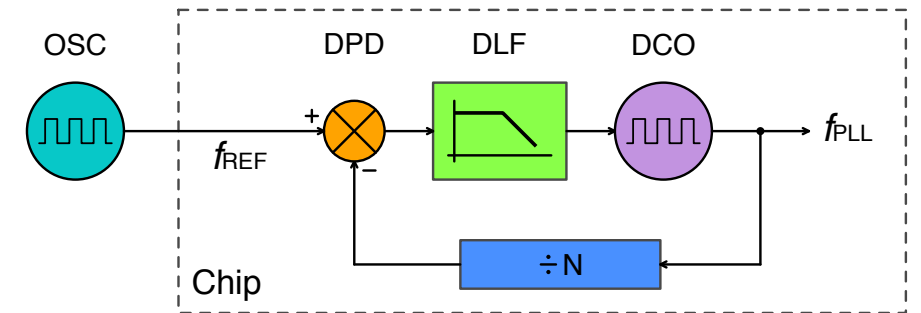

- What needs further explanation?
- How can we improve the DPD resolution?
- What makes the digital loop filter smaller than its analog counterpart?


Note: Digital filter design is a whole subject in itself!

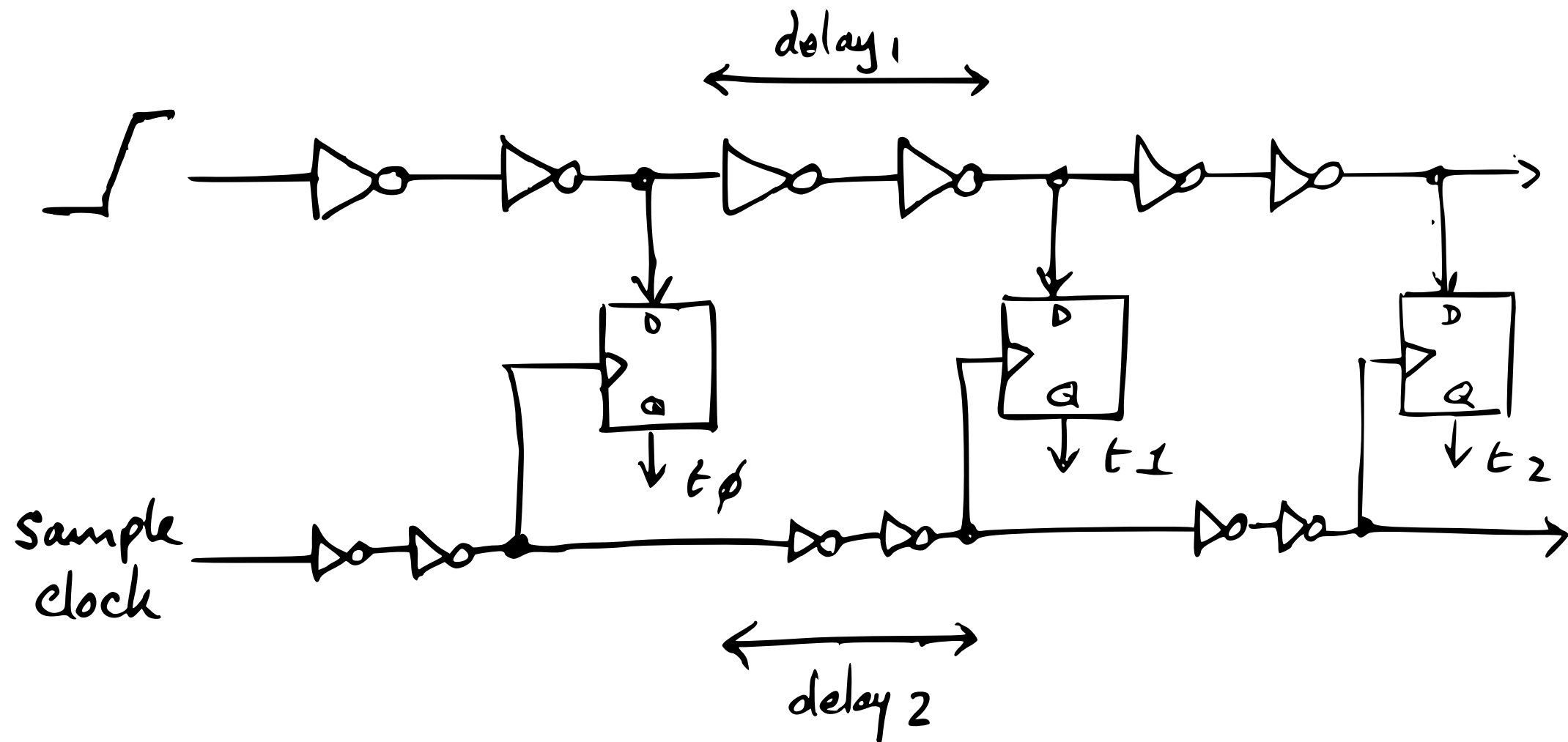Discussion Session #1: Vernier Tapped Delay Line




Do you see any possible problems?

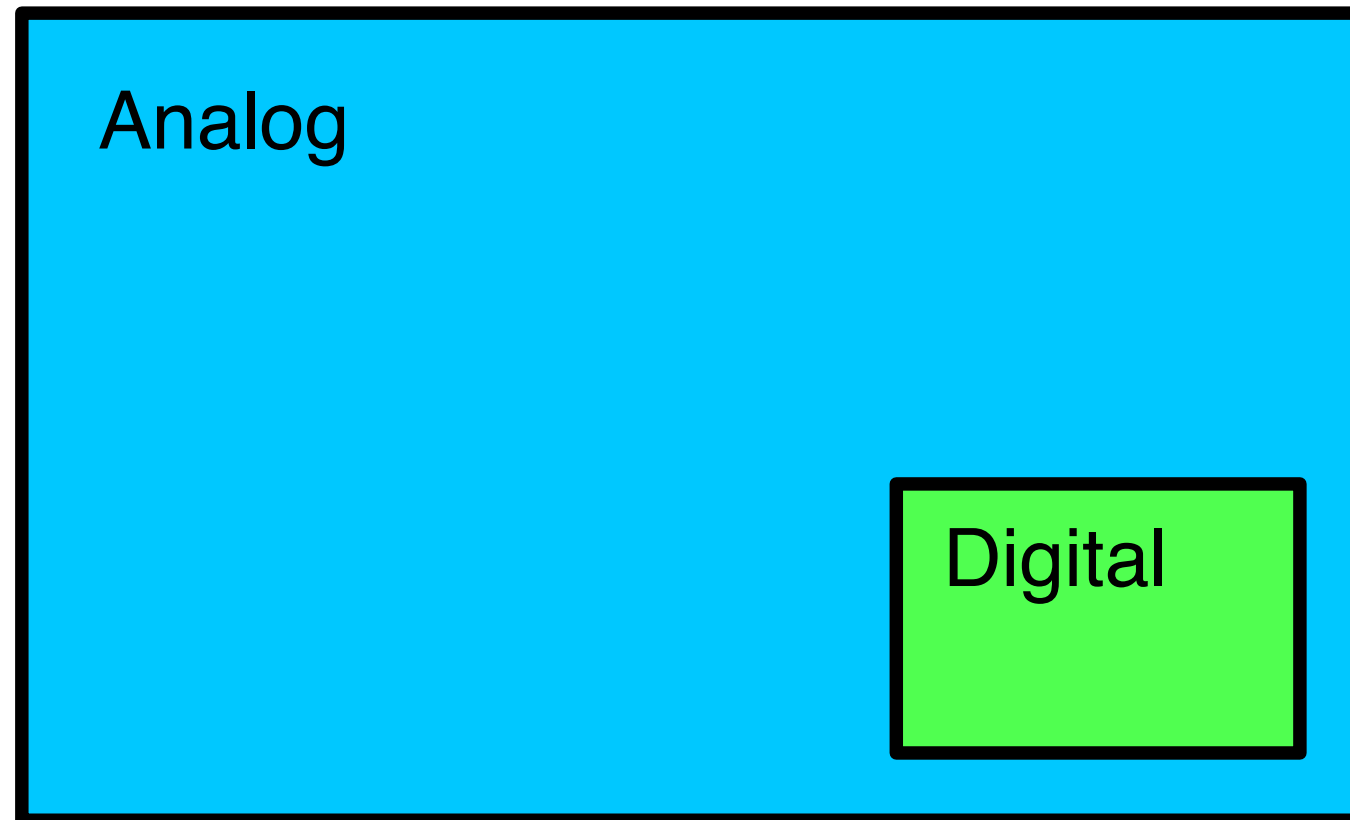Discussion Session #1: Digital loop filter size



Digital filter can be 10x smaller than analog filter:
large capacitances required by analog filter.

Discussion Session #1

 





END





Return to lecture

Outline



Part 1:

-  Overview
-  Intro to PLLs
-  Clocking with PLLs
-  Analog PLLs

Part 2:

-  Recap
-  Digital PLLs
-  **Future challenges**
-  Summary

Clocking Challenges

-  Gate delays becoming more sensitive to supply voltage variations
 - need to quickly adjust the clock to compensate
-  Cost of synchronization delays at clock domain crossings is too high
 - takes multiple clock cycles

Future



Future Chips



Technology advances bring:

- complete systems on chip
- more computing
- more clock domains
- more delay variation

Beyond PLLs


PLLs are so good!

Why are we fussing?

 -  PLLs are intentionally slow to respond to changes!
-  We require the clock frequency to adapt more rapidly to changes.





Future?

Rapid adjustment and tuning of clocks:







Outline

Part 1:

-  Overview
-  Intro to PLLs
-  Clocking with PLLs
-  Analog PLLs


Part 2:

-  Recap
-  Digital PLLs
-  Future challenges
-  Summary

Summary


- 🌐 PLLs are the greatest thing since sliced bread!
- 🌐 Stable & low jitter = more computing per clock cycle.
- 🌐 PLLs enable reliable data transfers.
- 🌐 Large power hungry circuits => move to digital PLLs.
- 🌐 Future needs:
 - responsive clock generators
 - clock tuning schemes

Discussion Session #2

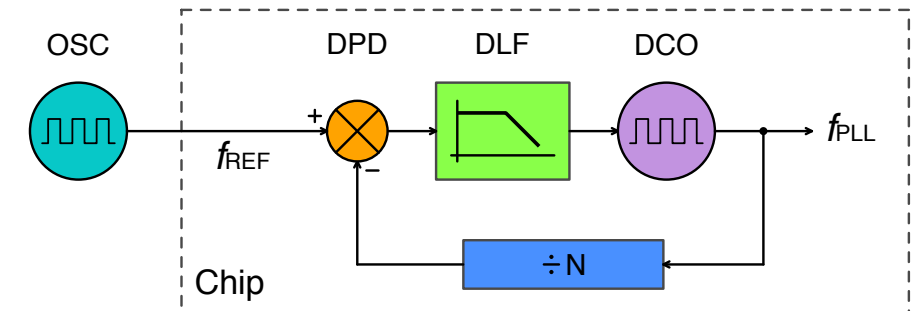

- What's not clear?
- Why have PLLs become the main way to generate on-chip clocks?
- Why are analog PLLs still the most common?
- Why are digital PLLs becoming popular?
- Other future needs?

Happy Holidays!

 

See you in 2021!